


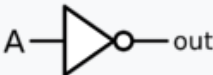


Chapter 11: Digital Electronics





WMC CS CLUB

April 7, 2022

§1 Digital Electronics

A digital circuit is constructed from logic gates. Each logic gate performs a function of boolean logic based on its inputs, such as AND or OR. Each circuit can be represented as a Boolean Algebra expression; this topic is an extension of the topic of Boolean Algebra, which includes a thorough description of truth tables and simplifying expressions.

NAME	GRAPHICAL SYMBOL	ALGEBRAIC EXPRESSION	TRUTH TABLE																		
BUFFER		$X = A$	<table><tr><th>INPUT</th><th>OUTPUT</th></tr><tr><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td></tr></table>	INPUT	OUTPUT	0	0	1	1												
INPUT	OUTPUT																				
0	0																				
1	1																				
NOT		$X = \overline{A}$ or $\neg A$	<table><tr><th>INPUT</th><th>OUTPUT</th></tr><tr><th>A</th><th>X</th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	INPUT	OUTPUT	A	X	0	1	1	0										
INPUT	OUTPUT																				
A	X																				
0	1																				
1	0																				
AND		$X = AB$ or $A \cdot B$	<table><tr><th colspan="2">INPUT</th><th>OUTPUT</th></tr><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	INPUT		OUTPUT	A	B	X	0	0	0	0	1	0	1	0	0	1	1	1
INPUT		OUTPUT																			
A	B	X																			
0	0	0																			
0	1	0																			
1	0	0																			
1	1	1																			
NAND		$X = \overline{AB}$ or $\overline{A \cdot B}$	<table><tr><th>INPUT</th><th>OUTPUT</th></tr><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	INPUT	OUTPUT	A	B	X	0	0	1	0	1	1	1	0	1	1	1	0	
INPUT	OUTPUT																				
A	B	X																			
0	0	1																			
0	1	1																			
1	0	1																			
1	1	0																			

OR		$X = A + B$	<table><tr><th colspan="2">INPUT</th><th>OUTPUT</th></tr><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	INPUT		OUTPUT	A	B	X	0	0	0	0	1	1	1	0	1	1	1	1
INPUT		OUTPUT																			
A	B	X																			
0	0	0																			
0	1	1																			
1	0	1																			
1	1	1																			
NOR		$X = \overline{A + B}$	<table><tr><th colspan="2">INPUT</th><th>OUTPUT</th></tr><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	INPUT		OUTPUT	A	B	X	0	0	1	0	1	0	1	0	0	1	1	0
INPUT		OUTPUT																			
A	B	X																			
0	0	1																			
0	1	0																			
1	0	0																			
1	1	0																			
XOR		$X = A \oplus B$	<table><tr><th colspan="2">INPUT</th><th>OUTPUT</th></tr><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	INPUT		OUTPUT	A	B	X	0	0	0	0	1	1	1	0	1	1	1	0
INPUT		OUTPUT																			
A	B	X																			
0	0	0																			
0	1	1																			
1	0	1																			
1	1	0																			
XNOR		$X = \overline{A \oplus B}$ or $A \odot B$	<table><tr><th colspan="2">INPUT</th><th>OUTPUT</th></tr><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	INPUT		OUTPUT	A	B	X	0	0	1	0	1	0	1	0	0	1	1	1
INPUT		OUTPUT																			
A	B	X																			
0	0	1																			
0	1	0																			
1	0	0																			
1	1	1																			


§2 Online Tools

The ACSL proposes the Logisim (<http://www.cburch.com/logisim/index.html>) application for digital electronics experimentation. Logisim is a wonderful tool for exploring this topic. Logisim is free to download and use; among its many features is support to automatically draw a circuit from a Boolean Algebra expression; to simulate the circuit with arbitrary inputs; and to complete a truth table for the circuit.


§3 Practice Problems

§3.1 Problems

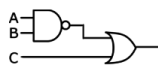
- Find all ordered triplets (A, B, C) which make the following circuit FALSE:



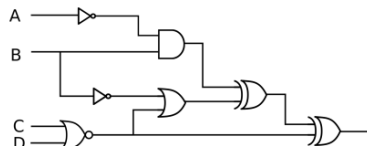- How many ordered 4-tuples (A, B, C, D) make the following circuit TRUE?



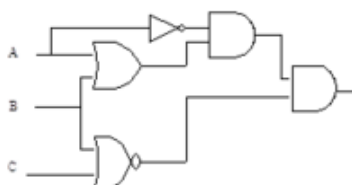- Simplify the Boolean expression that this circuit represents.



§3.2 Answer Key

- For the circuit to be FALSE, both inputs to the OR gate must be false. Thus, input C must be FALSE, and the output of the NAND gate must also be false. The NAND gate is false only when both of its inputs are TRUE; thus, inputs A and B must both be TRUE. The final answer is (TRUE, TRUE, FALSE), or **(1, 1, 0)**.
- We'll use a truth table to solve this problem. The rows in the truth table will correspond to all possible inputs - 16 in this case, since there are 4 inputs. From the truth table, there are **10** rows where the final output is TRUE.
- The circuit can be simplified to **0**, or always false.